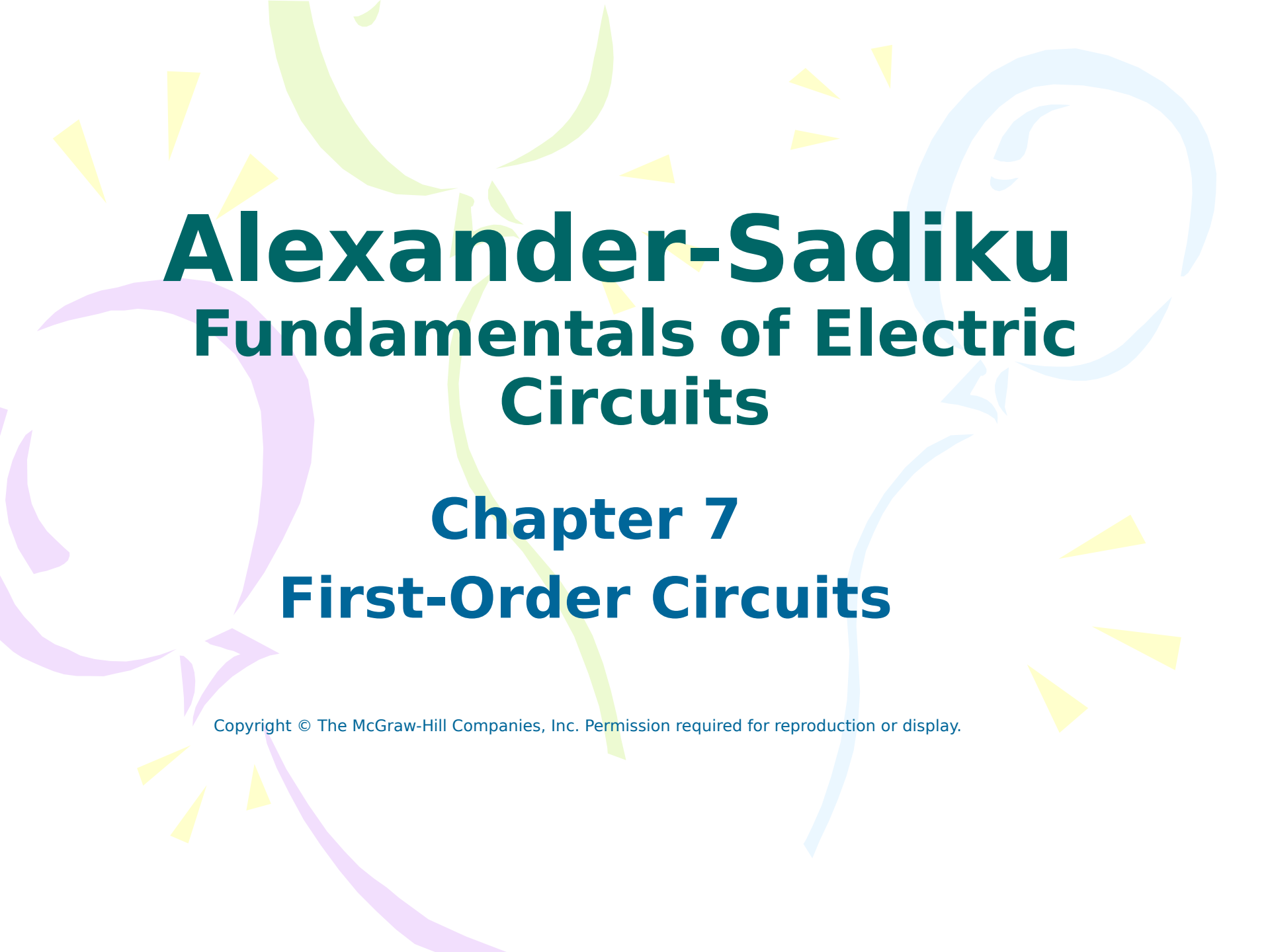


The background features several large, overlapping, curved shapes in light green, light blue, and light purple. Scattered throughout are numerous small, yellow, triangular shapes, some pointing upwards and others downwards, creating a festive or celebratory feel.


Alexander-Sadiku

Fundamentals of Electric Circuits

Chapter 7

First-Order Circuits

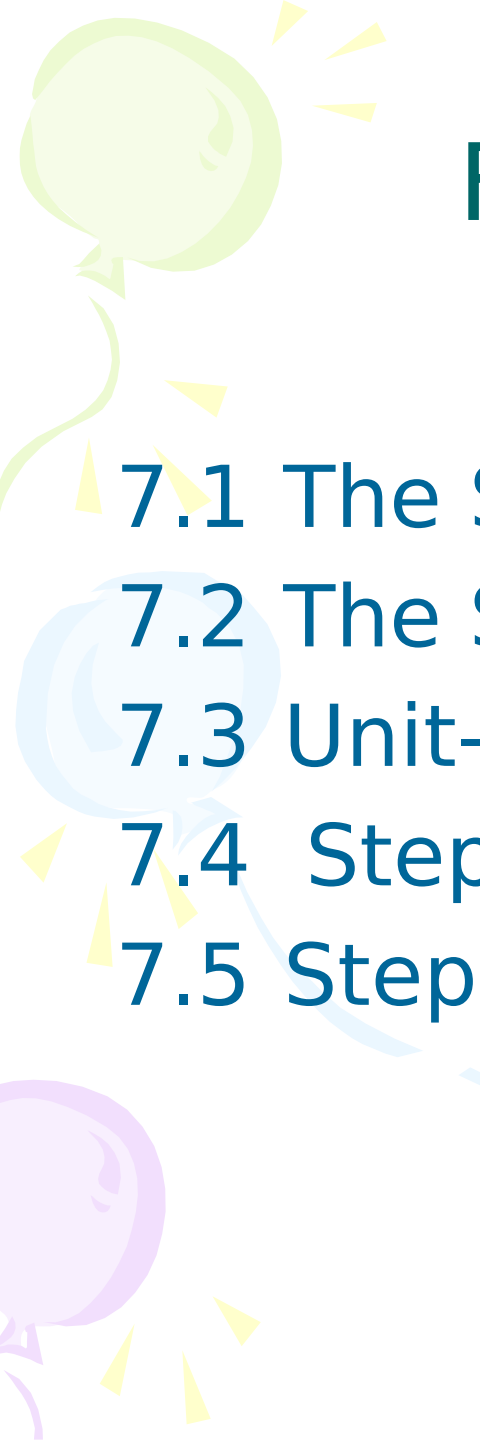Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



First-Order Circuits

Chapter 7

7.1 The Source-Free RC Circuit

7.2 The Source-Free RL Circuit


7.3 Unit-step Function

7.4 Step Response of an RC Circuit

7.5 Step Response of an RL Circuit

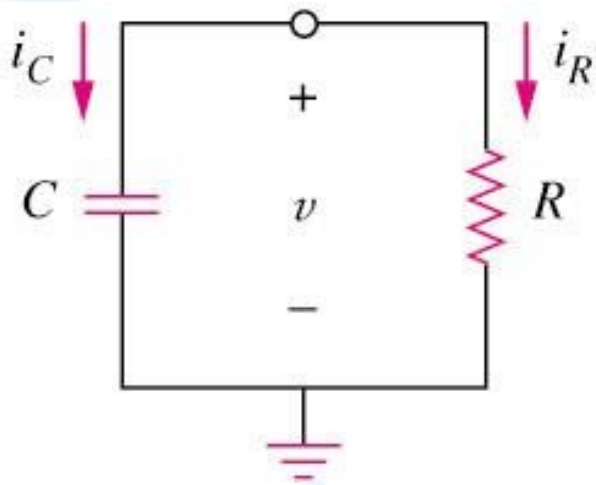7.1 The Source-Free RC Circuit (1)

- A **first-order circuit** is characterized by a first-order differential equation.



By KCL

$$i_R + i_C = 0 \rightarrow \frac{v}{R} + C \frac{dv}{dt} = 0$$



Ohms law

Capacitor law

- Apply Kirchhoff's laws to purely resistive circuit results in algebraic equations.
- Apply the laws to RC and RL circuits produces differential equations.

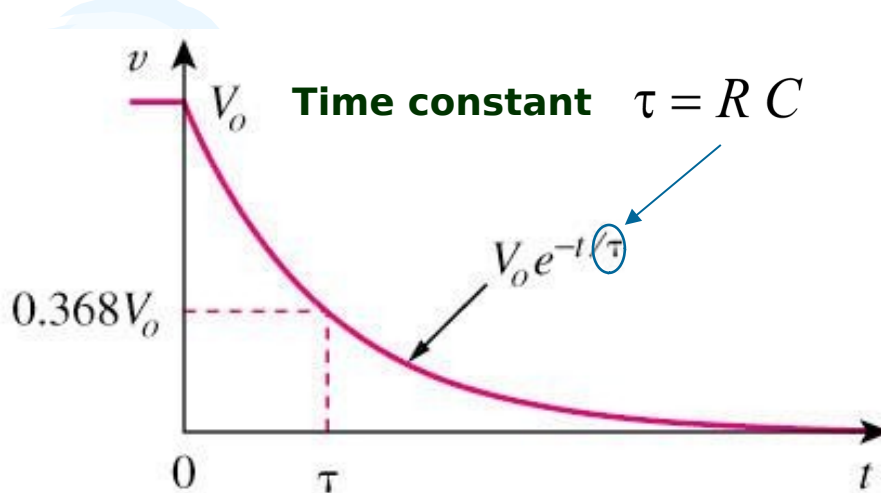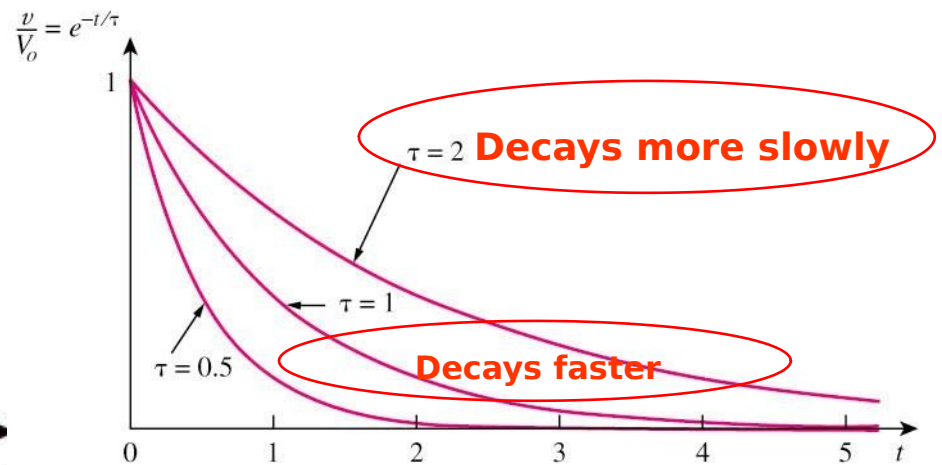7.1 The Source-Free RC Circuit (2)

- The **natural response** of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.




- The **time constant** τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- v decays **faster** for small τ and **slower** for large τ .

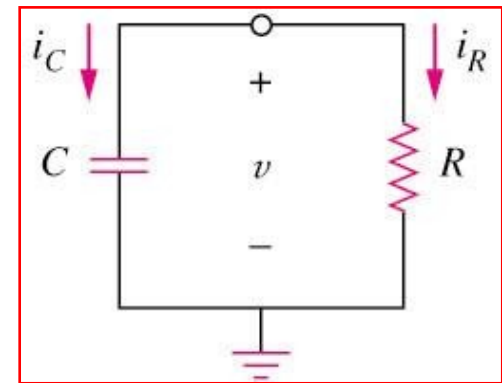7.1 The Source-Free RC Circuit (3)

The key to working with a source-free RC circuit is finding:

$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = R C$$




1. The initial voltage $v(0) = V_0$ across the capacitor.
2. The time constant $\tau = RC$.

7.1 The Source-Free RC Circuit (4)

Example 1

Refer to the circuit below, determine v_C , v_x , and i_o for $t \geq 0$.

Assume that $v_C(0) = 30$ V.

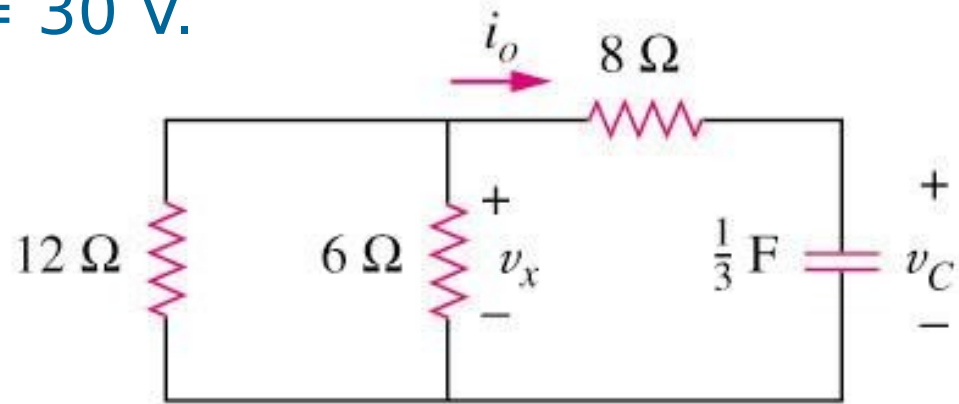


- Please refer to lecture or textbook for more detail elaboration.

Answer: $v_C = 30e^{-0.25t}$ V ; $v_x = 10e^{-0.25t}$; $i_o = -2.5e^{-0.25t}$ A

7.1 The Source-Free RC Circuit (5)

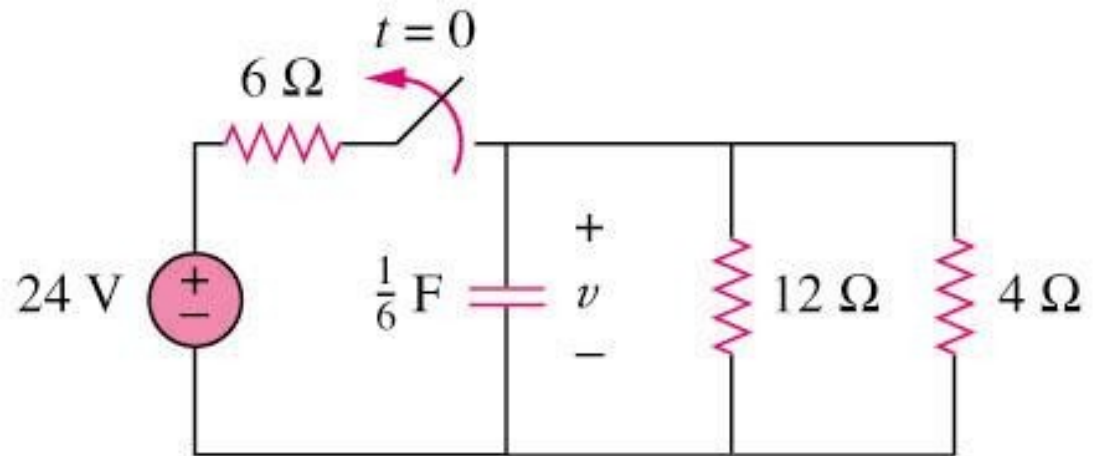Example 2

The switch in circuit below is opened at $t = 0$, find $v(t)$ for $t \geq 0$.




- Please refer to lecture or textbook for more detail elaboration.

Answer: $V(t) = 8e^{-2t} \text{ V}$

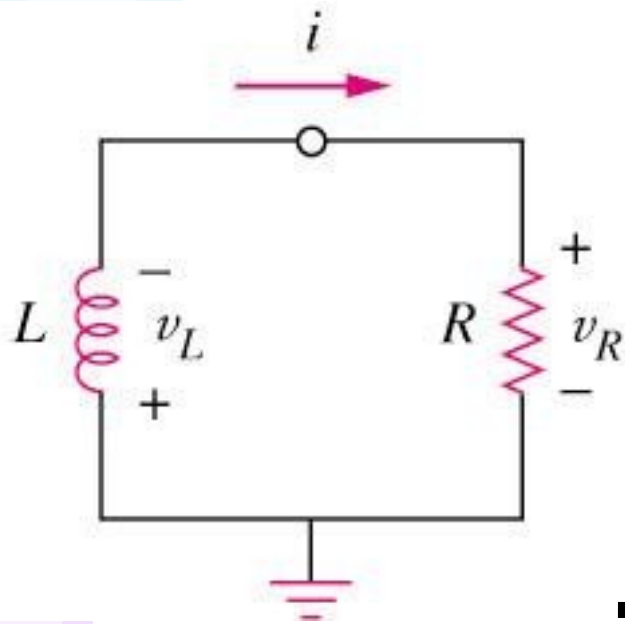7.2 The Source-Free RL Circuit (1)

- A **first-order RL circuit** consists of a inductor L (or its equivalent) and a resistor (or its equivalent)




By KVL $v_L + v_R = 0$

$\rightarrow L \frac{di}{dt} + iR = 0$

Inductors law Ohms law

$\rightarrow \frac{di}{i} = -\frac{R}{L} dt \rightarrow i(t) = I_0 e^{-Rt/L}$

7.2 The Source-Free RL Circuit (2)

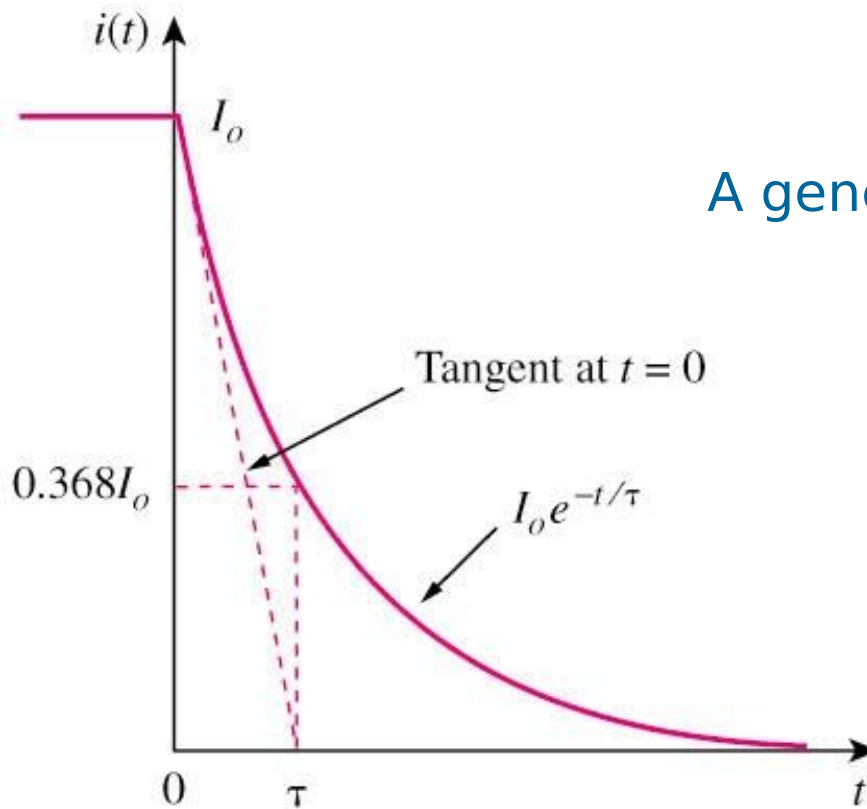

A general form representing a RL

$$i(t) = I_0 e^{-t/\tau}$$

where $\tau = \frac{L}{R}$


- The **time constant** τ of a circuit is the time required for the response to decay by a factor of $1/e$ or 36.8% of its initial value.
- $i(t)$ decays **faster** for small τ and **slower** for large τ .
- The general form is very similar to a RC source-free circuit.

7.2 The Source-Free RL Circuit (3)

Comparison between a RL and RC circuit


A RL source-free circuit
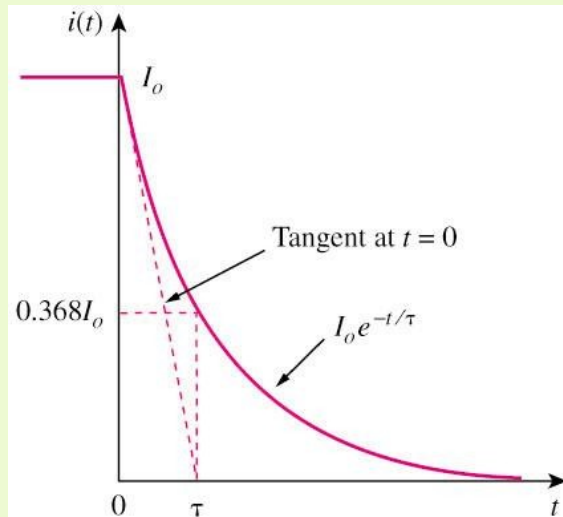
$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$



A RC source-free circuit

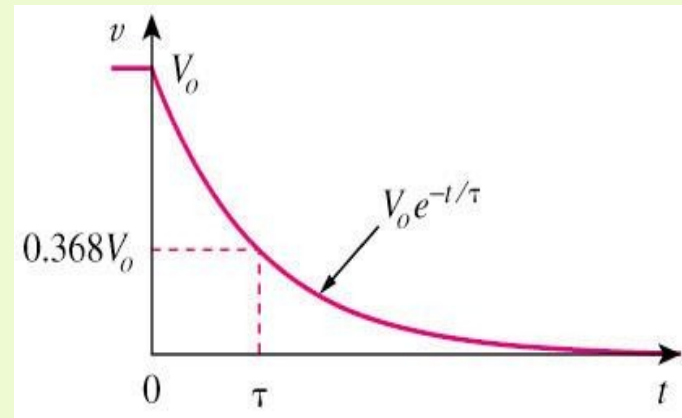
$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$



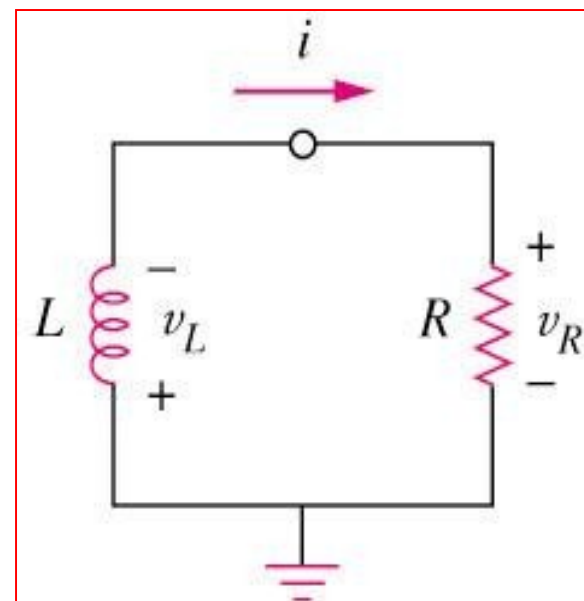7.2 The Source-Free RL Circuit (4)

The key to working with a source-free RL circuit is finding:

$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$




1. The initial voltage $i(0) = I_0$ through the inductor.
2. The time constant $\tau = L/R$.

7.2 The Source-Free RL Circuit (5)

Example 3

Find i and v_x in the circuit.

Assume that $i(0) = 5$ A.

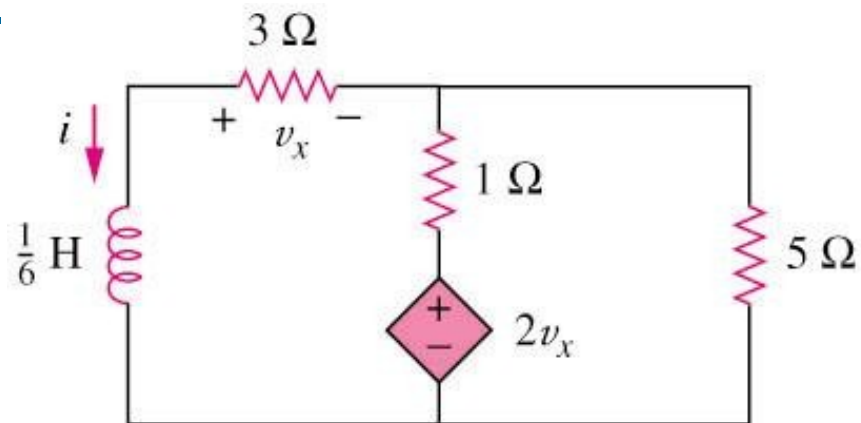


- Please refer to lecture or textbook for more detail elaboration.

Answer: $i(t) = 5e^{-53t}$ A

7.2 The Source-Free RL Circuit (6)

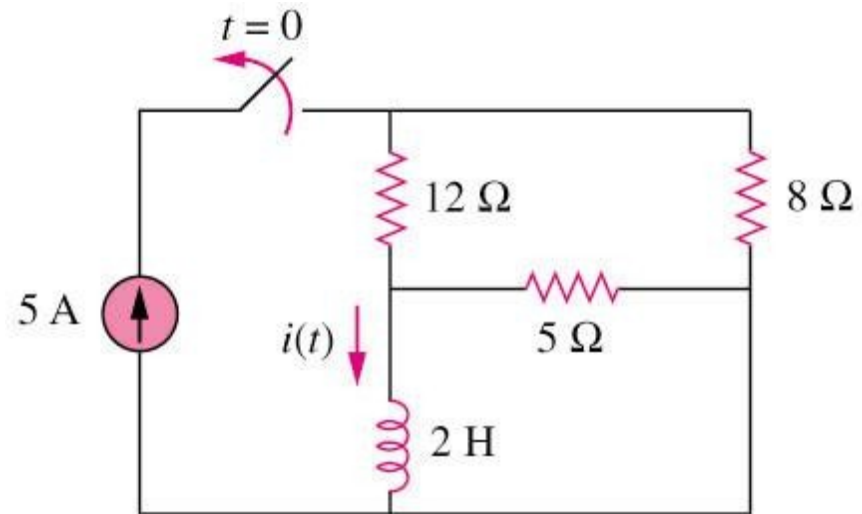Example 4

For the circuit, find $i(t)$ for $t > 0$.




- Please refer to lecture or textbook for more detail elaboration.

Answer: $i(t) = 2e^{-2t}\ \text{A}$

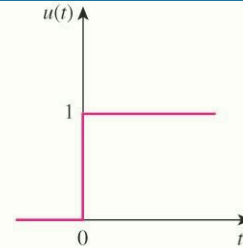
7.3 Unit-Step Function (1)

- The **unit step function** $u(t)$ is 0 for negative values of t and 1 for positive values of t .


$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


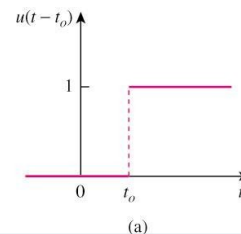
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



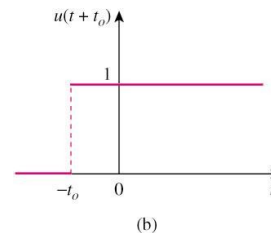
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




7.3 Unit-Step Function (2)

Represent an abrupt change for:

1. voltage source.

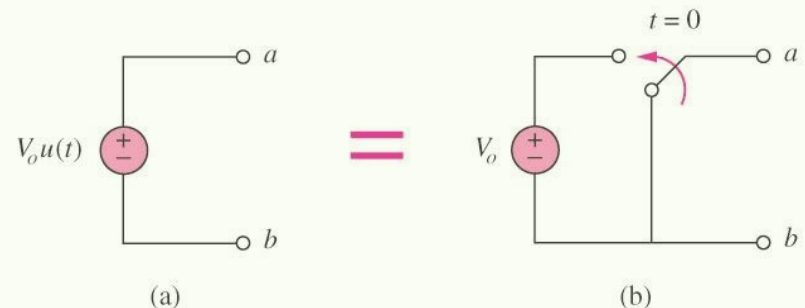


2. for current source:

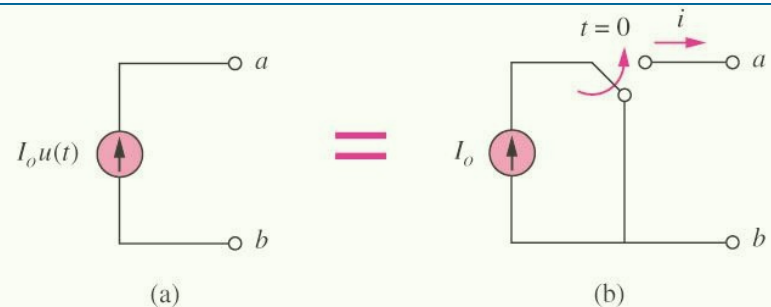

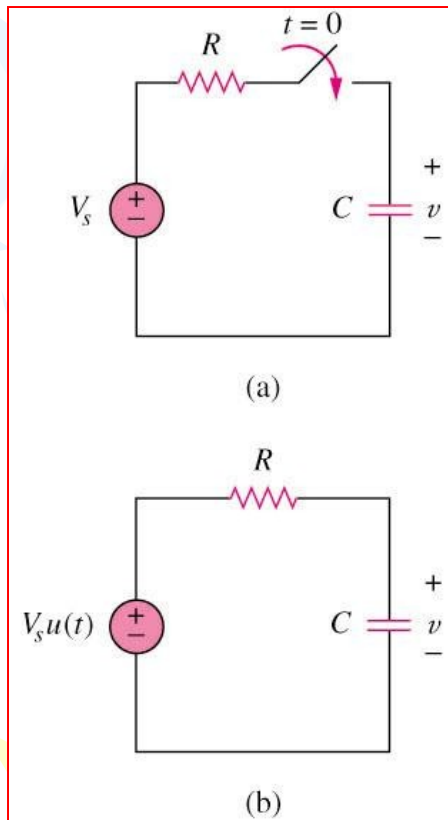7.4 The Step-Response of a RC Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial condition:**

$$v(0^-) = v(0^+) = V_0$$

- Applying KCL,

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$


or

$$\frac{dv}{dt} = -\frac{v - V_s}{RC} u(t)$$

- Where $u(t)$ is the unit-step function

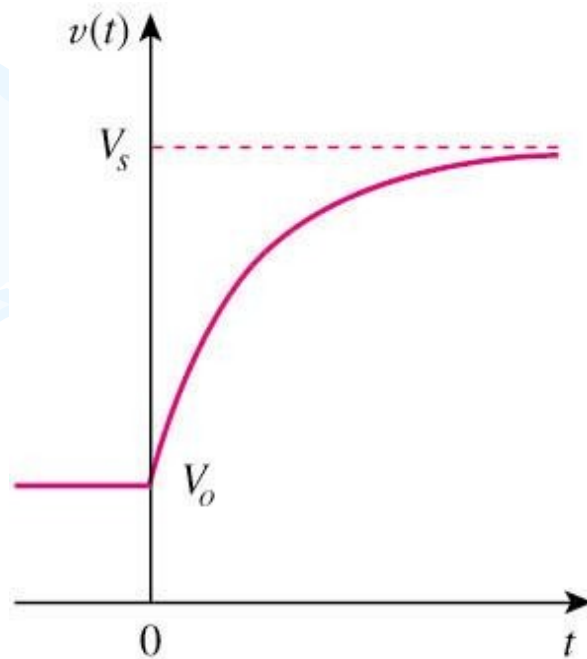7.4 The Step-Response of a RC Circuit (2)

- Integrating both sides and considering the initial conditions, the solution of the equation is:



$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

Final value at $t \rightarrow \infty$ Initial value at $t = 0$ Source-free Response

$$\begin{aligned} \text{Complete Response} &= \text{Natural response (stored energy)} + \text{Forced Response (independent source)} \\ &= V_0 e^{-t/\tau} + V_s (1 - e^{-t/\tau}) \end{aligned}$$

7.4 The Step-Response of a RC Circuit (3)

Three steps to find out the step response of an RC circuit:

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$ — DC voltage across C.
3. The time constant τ .

$$v(t) = v(\infty) + [v(0+) - v(\infty)]e^{-t/\tau}$$


Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

7.4 The Step-Response of a RC Circuit (4)

Example 5

Find $v(t)$ for $t > 0$ in the circuit in below. Assume the switch has been open for a long time and is closed at $t = 0$.

Calculate $v(t)$ at $t = 0.5$.

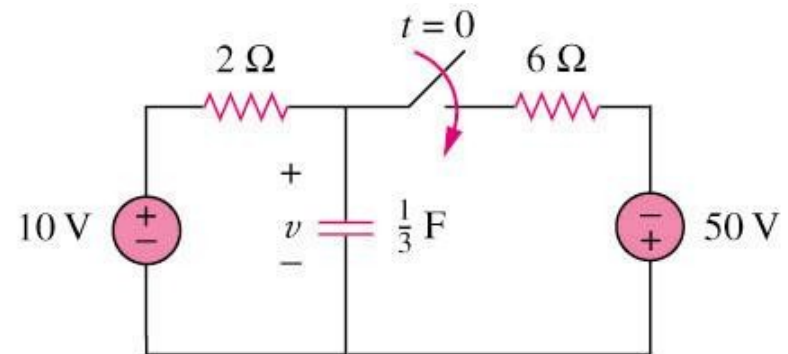


- Please refer to lecture or textbook for more detail elaboration.

Answer: $v(t) = 15e^{-2t}$ and $v(0.5) = 0.5182V$

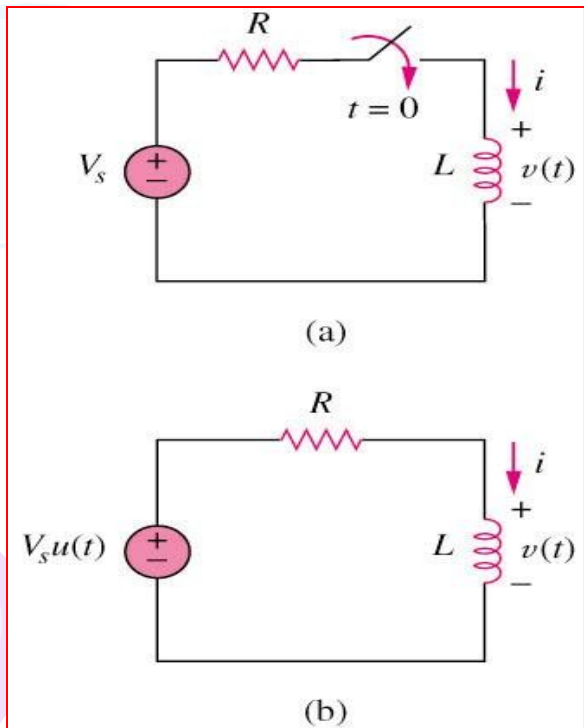7.5 The Step-response of a RL Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial current**
 $i(0^-) = i(0^+) = I_o$
- Final inductor current**
 $i(\infty) = V_s/R$
- Time constant $\tau = L/R$

$$i(t) = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R}\right) e^{-\frac{t}{\tau}} u(t)$$

7.5 The Step-Response of a RL Circuit (2)

Three steps to find out the step response of an RL circuit:

1. The initial inductor current $i(0)$ at $t = 0+$.
2. The final inductor current $i(\infty)$.
3. The time constant τ .

$$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau}$$


Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor V-I laws.

7.5 The Step-Response of a RL Circuit (4)

Example 6

The switch in the circuit shown below has been closed for a long time. It opens at $t = 0$.

Find $i(t)$ for $t > 0$.

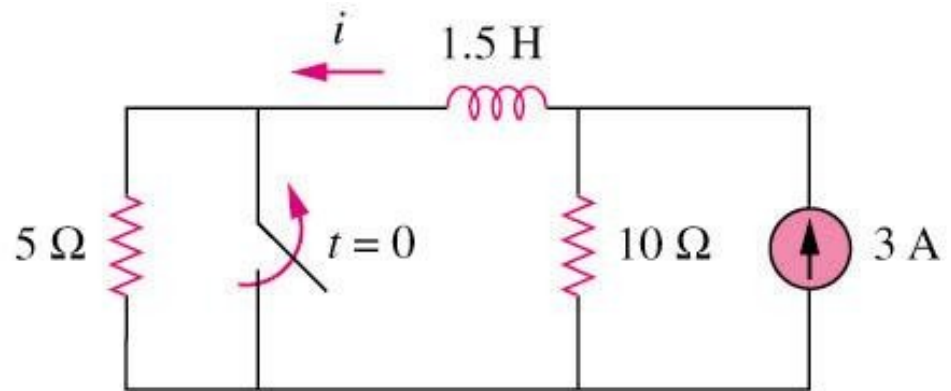

- Please refer to lecture or textbook for more detail elaboration.

Answer: $i(t) = 2 + e^{-10t}$