Hill Side School

Score	%
Tests	
Final	
Others	
Total	

Excel with our support

Central Administrative office (CMC Campus)
Primary Division Phone 011-646 69 40
High School Division Phone 011-646 36 88
Lem Campus (Lem Hotel Area)
Primary Division Phone 011-662 4
KG Campus (Koteba Area)
Kindergarten Division Phone 011-645 74 44

P.O.Box 21616 Addis Ababa, Ethiopia

@ ethionet.et

Parent's Signature

Full Name: _____ Grade: 6 Section: _____

Subject: Science Year: 2012 E.C work

General instruction: attempt all the questions.

1. Write the safety measure to be taken while operating electrical device.

_____

_____

2. Draw a diagram of parallel circuit.

_____

_____

3. What is the use electric wire or cable?

_____

_____

4. Which kind of circuit has a branch?

_____

_____

5. What is difference between closed circuit and opened circuit?

_____

_____

6. Give two examples of insulating or non- conducting materials.

_____

_____

7. List some component of electric bulb.

_____

_____

8. Give three examples of conducting materials.

_____

_____

9. Define what electric circuit means.

_____

_____

10. List four sources of electricity

_____

_____